



# Mini Project 2

ELEC 301

[pgoel125@student.ubc.ca](mailto:pgoel125@student.ubc.ca)  
90300815

## Contents

Introduction.....	1
Problems .....	2
PART 1 .....	2
PART 2 .....	6
PART 3 .....	11
Conclusion .....	13
References.....	14

## Table of Circuits

Circuit 1 .....	2
Circuit 2 .....	3
Circuit 3 .....	3
Circuit 4: Bias Network for npn transistor .....	4
Circuit 5: 1/3 Rule Bias .....	5
Circuit 6: Bias Circuit for 2N3904 and 2N4401 .....	6
Circuit 7: Common Emitter Amplifier .....	6
Circuit 8: High frequency small-signal model .....	7
Circuit 9: Common Base Amplifier .....	11

## Table of Plots

Plot 1: $I_B$ v/s $V_{BE}$ .....	2
Plot 2: $I_C$ v/s $V_{CE}$ with variable $I_{BN}$ .....	3
Plot 3: $I_C$ v/s $V_{CE}$ with variable $V_{BE}$ .....	3
Plot 4: Phase (degrees) Bode Plot .....	7
Plot 5: Magnitude Bode Plot .....	7
Plot 6: Linear Interpolation for Measuring poles and zeros .....	8
Plot 7: Phase Bode Plot for 2N4401 .....	8
Plot 8: Magnitude Bode Plot for 2N4401 .....	8
Plot 9: Transfer Curve for 2N4401 .....	9
Plot 10: Transfer Curve for 2N3904 .....	9
Plot 11: Phase Bode Plot for CB Amplifier .....	11
Plot 12: Magnitude Bode Plot for CB Amplifier .....	11
Plot 13: Transfer Curve for 2N2222A .....	12

## Introduction

The aim of this project report is to detail the modeling of bipolar junction transistors that are intended for small signal operation using a hybrid- $\pi$  model. Specifically, two basic single transistor amplifier circuits, namely the common emitter and common base amplifiers, will be examined. It is important to note that the analysis is conducted under the assumption of small signals, as larger signals can cause the transistors to enter saturation or cut-off modes, where the hybrid- $\pi$  model is no longer applicable. The project employs three different types of transistors, namely 2N2222A, 2N3904, and 2N4401, and their datasheets were sourced from the manufacturers' websites.

## Problems

### PART 1


#### A. Small Signal Parameters

The values of the small signal parameters for  $V_{CE} = 10V$ ,  $I_C = 1\text{ mA}$ ,  $f = 1\text{ kHz}$  and  $T = 25^\circ\text{C}$  are,


Parameter	Min	Max
$h_{fe}$	50	300
$h_{ie}$	2 k $\Omega$	8 k $\Omega$
$h_{oe}$	5 $\mu\text{S}$	35 $\mu\text{S}$

#### B. Calculation of hybrid- $\pi$ Model Parameters


Using *CircuitMaker* and the Circuits given below to plat the graphs to obtain the values

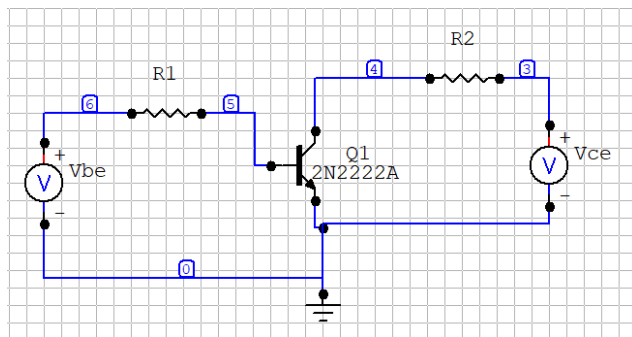


Circuit 1

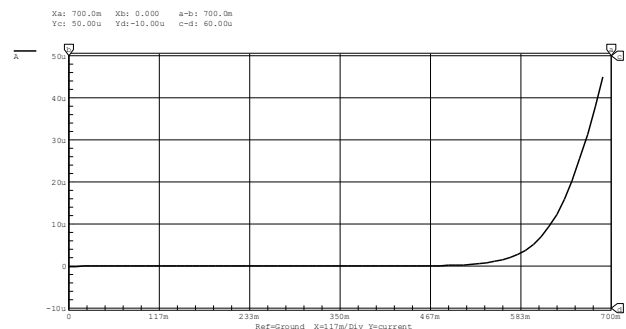

Plot 1:  $I_B$  v/s  $V_{BE}$

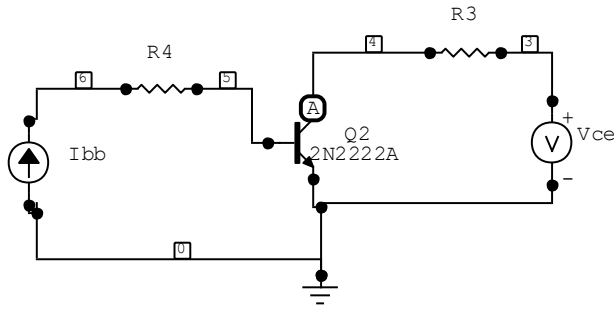


Circuit 2

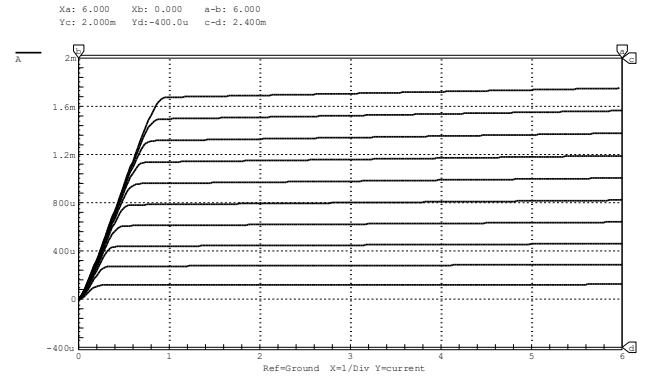


Plot 2:  $I_C$  v/s  $V_{CE}$  with variable  $I_{B\text{N}}$

In  $I_C$  vs  $V_{CE}$  plot, variable  $I_B = 1\mu\text{A}$  increments, with top increment  $I_B = 10\mu\text{A}$ .

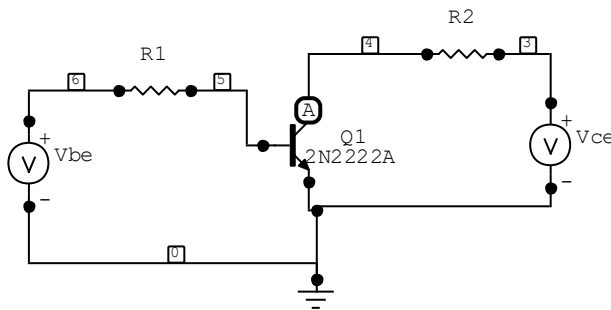

Circuit 3

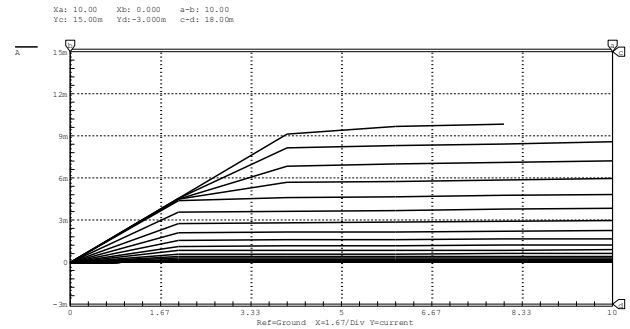

Plot 3:  $I_C$  v/s  $V_{CE}$  with variable  $V_{BE}$

For the calculation of  $\beta$ ,  $r_\pi$ ,  $g_m$ , and  $r_o$  for  $V_{CE} = 5\text{ V}$  and  $I_C = 1\text{ mA}$ .

From Plot 2, at given data  $I_B = 6\mu\text{A}$ . Since  $I_C = \beta I_B$ ,

$$\beta = 166.7$$

$$g_m = \frac{I_C}{V_T} = \frac{1\text{ mA}}{25\text{ mV}} = 0.040\text{ S} \quad | \text{ Given that } V_T = 25\text{ mV at } T = 25^\circ\text{C}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{166.7}{0.040} = 4167\Omega$$


Next, for  $r_o$  we can estimate  $V_A$  by calculating the slope of active region at  $I_B = 8\mu\text{A}$

$$m_{8\mu\text{A}} = \frac{(1.4207 - 1.327)\text{ mA}}{(8.333 - 1.667)\text{ V}} = \frac{(1.4207 - 0)\text{ mA}}{(8.333 - V_A)\text{ V}}, \text{ Therefore } V_A = -108.922\text{ V}$$

$$\text{Thus } r_o = \frac{V_A}{I_C} = \frac{108.922\text{ V}}{1\text{ mA}} = 108.922\text{ k}\Omega$$

$$V_{BE} = 0.6 \text{ V}$$

	$\beta$	$r_{\pi}$	$g_m$
<b>Measured</b>	166.7	4.167 k $\Omega$	0.040
<b>Datasheet (Mean Values)</b>	175	4.375 k $\Omega$	0.040

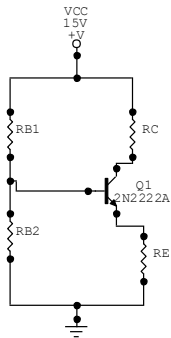

### C. Bias Network

i. Values of all the currents:

$$I_C = 1 \text{ mA}; I_B = \frac{I_C}{\beta} = 6 \mu\text{A}; I_E = I_C + I_B = 1.006 \text{ mA}$$

Mesh Analysis from  $V_{CC}$  to ground, ( $V_{CE} = 4 \text{ V}$ )

$$15 = I_C R_C + V_{CE} + I_E R_E$$

$$15 - 4 = (1 \text{ mA}) R_C + 1.006 \text{ mA} \left( \frac{1}{2} R_C \right)$$

$$R_C = 7318.6959 \Omega$$

$$R_E = 3659.3479 \Omega$$

Circuit 4: Bias Network for npn transistor

$$\text{Hence, } V_E = R_E I_E = 3.6593 \text{ V}; V_C = V_E + V_{CE} = 7.6593 \text{ V}; V_B = V_E + V_{BE} = 4.4593 \text{ V}$$

$$\text{To find } R_{B1} \text{ and } R_{B2}, V_{CC} = V_B + R_{B1} I_1; V_B = R_{B2} I_2, \text{ and } I_1 = I_B + I_2$$

Choosing  $R_{B1} = 1 \text{ M}\Omega$ ;  $R_{B2} = 939.362 \text{ k}\Omega$ , Since solving Equations is not Linear.

$I_C$	$I_B$	$I_E$	$V_C$	$V_B$	$V_E$
<b>1.009 mA</b>	6.091	1.105 mA	7.61	4.315	3.714

i. Biasing using 1/3 Rule

$$V_B = \frac{1}{3} V_{CC} = 5 \text{ V}; V_C = \frac{2}{3} V_{CC} = 10 \text{ V and } I_1 = \frac{I_E}{\sqrt{\beta}}$$

$$V_E = V_B - V_{BE} = 4.4 \text{ V}$$

Current Values,

$$I_C = 1 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = 6 \mu\text{A}$$

$$I_E = I_C + I_B = 1.006 \text{ mA}$$

$$I_2 = I_1 - I_B = \frac{1.006 \text{ mA}}{\sqrt{166.7}} - 0.006 \text{ mA} = 71.9166 \mu\text{A}$$


Resistance Values

$$R_C = \frac{V_{CC}}{I_C} = \frac{5 \text{ V}}{1 \text{ mA}} = 5 \text{ k}\Omega$$

$$R_E = \frac{V_E}{I_E} = \frac{4.3}{1.006} = 4.274 \text{ k}\Omega$$

$$R_{B1} = \frac{V_{CC} - V_B}{I_1} = \frac{10}{77.917} = 128.342 \text{ k}\Omega$$

$$R_{B2} = \frac{V_B}{I_2} = \frac{5}{71.92} = 69.524 \text{ k}\Omega$$

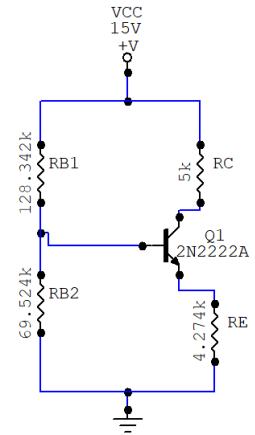

Circuit 5: 1/3 Rule Bias

DC operating point values (Values are measured in *CircuitMaker*) :

I <sub>C</sub>	I <sub>B</sub>	I <sub>E</sub>	V <sub>c</sub>	V <sub>B</sub>	V <sub>E</sub>
1.024 mA	6.097 μA	1.030 mA	9.889 V	4.996 V	4.395 V


## ii. Using standard Resistor Values

R <sub>B1</sub>	R <sub>B2</sub>	R <sub>C</sub>	R <sub>E</sub>
130 kΩ	68 kΩ	5.1 kΩ	4.3 kΩ

I <sub>C</sub>	I <sub>B</sub>	I <sub>E</sub>	V <sub>c</sub>	V <sub>B</sub>	V <sub>E</sub>
0.991 mA	5.927 μA	0.997 mA	9.946 V	4.888 V	4.1888 V

iii. On comparison, the values of dc operating points are very similar. But the 1/3 rule is most efficient since it is easy to calculate.

ii. **DC Operating points for 2N3904 and 2N4401**

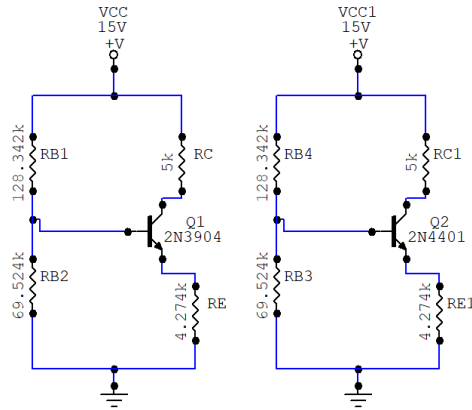


*Circuit 6: Bias Circuit for 2N3904 and 2N4401*

Using Similar Method and *CircuitMaker* the following values for 2N3904 and 2N4401 are:


	$I_C$	$I_B$	$I_E$	$V_C$	$V_B$	$V_E$
<b>2N3904</b>	0.986 mA	8.314 $\mu$ A	0.994 mA	10.07 V	4.896 V	4.250 V
<b>2N4401</b>	1.003 mA	6.791 $\mu$ A	1.010 mA	9.995 V	4.965 V	4.307 V
<b>2N2222A</b>	0.991 mA	5.927 $\mu$ A	0.997 mA	9.946 V	4.888 V	4.1888 V

**PART 2**

A.

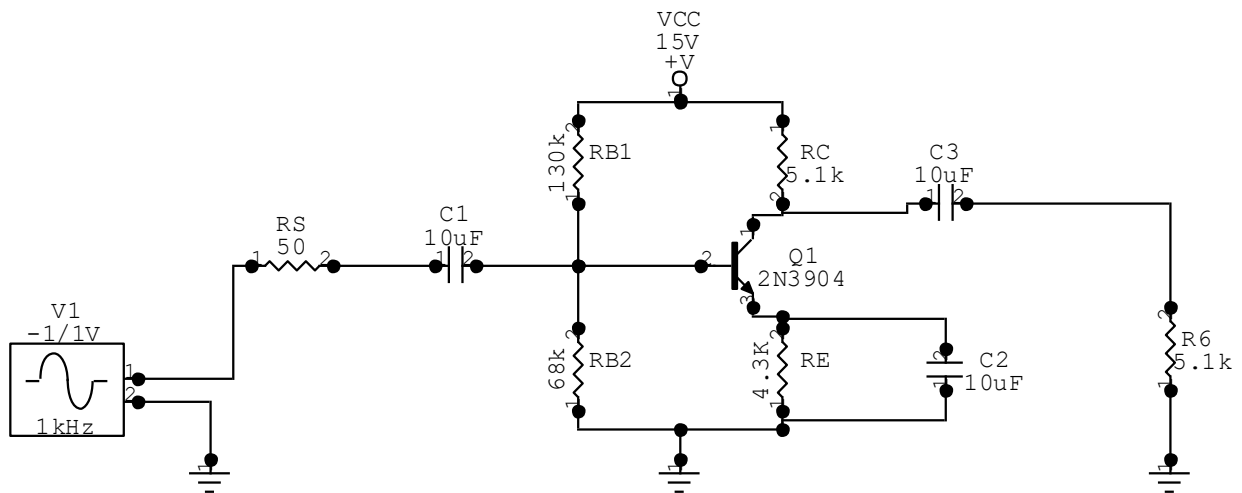

*Circuit 7: Common Emitter Amplifier*

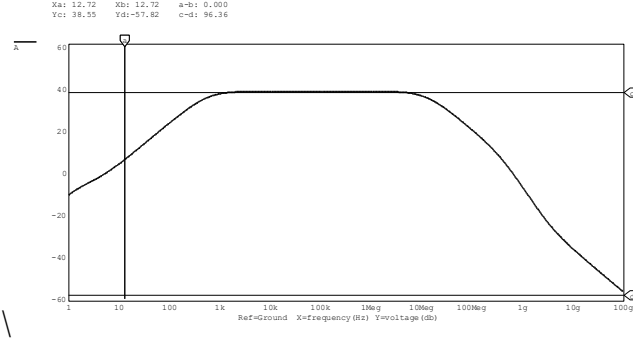

Plot 5: Magnitude Bode Plot

$$g_m = \frac{956.1 \mu A}{0.025 V} = 0.03824 S$$

$$V_{CB} = 10.12 - 4.790 = 5.330 V$$


$$V_{BE} = 4.79 - 4.145 = 0.645 V$$

$$C_\pi \approx 2 * C_{JE} + T_F * g_m = 24.2976 pF$$

$$C_\mu \approx \frac{C_{JC}}{\left(1 + \frac{V_{CB}}{V_{JC}}\right)^{M_{JC}}} = 1.7545 pF$$

$$k = -g_m(R_C || R_L) = -102$$

$$r_\pi = 3.08 k\Omega$$

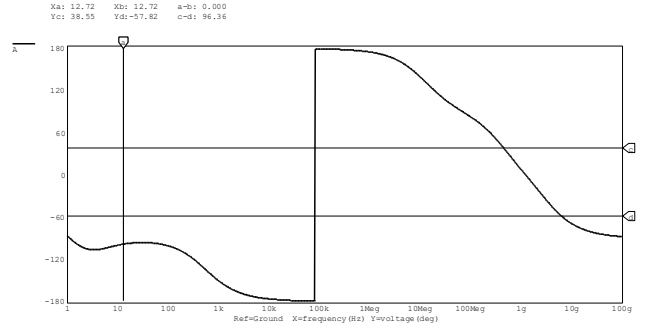


Plot 4: Phase (degrees) Bode Plot

$$\omega_{LZ3} = \frac{1}{R_E C_E} = 3.7013 Hz$$

$$\omega_{LP1} = \frac{1}{C_1(R_S + (R_E(1 + \beta) + r_\pi) || R_{BB})} = 0.3873 Hz$$

$$\omega_{LP2} = \frac{1}{(R_L + R_C)C_2} = 1.5603 Hz$$

$$\omega_{LP3} = \frac{1}{\left(R_E || \frac{R_{BB} || R_S + r_\pi}{1 + \beta}\right) C_1} = 635.278 Hz$$

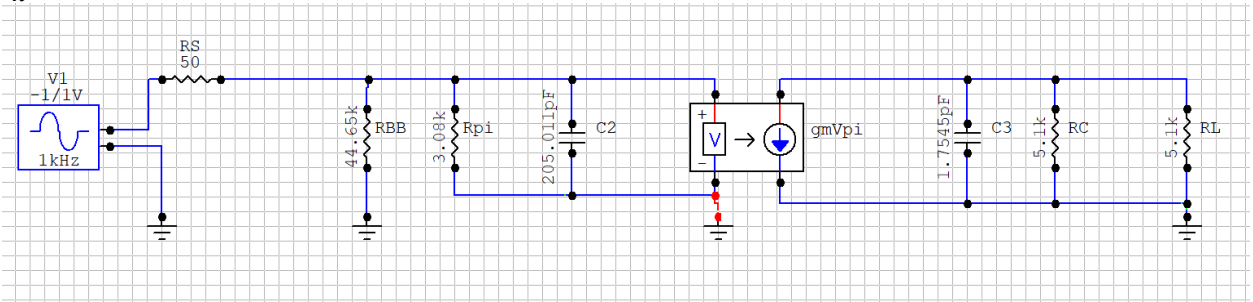

Circuit 8: High frequency small-signal model

$$C_2 = C_\pi + C_\mu(1 - k)$$

$$C_3 = C_\mu$$


$$\omega_{HP1} = \frac{1}{(R_{BB} || R_S || r_\pi) C_2} = 15.7959 MHz$$

$$\omega_{HP2} = \frac{1}{(R_L || R_C) C_\mu} = 34.3839 MHz$$



↓


Xa: 12.72 Xb: 12.72 a-b: 0.000  
Yc: 38.55 Yd: -57.82 c-d: 96.36

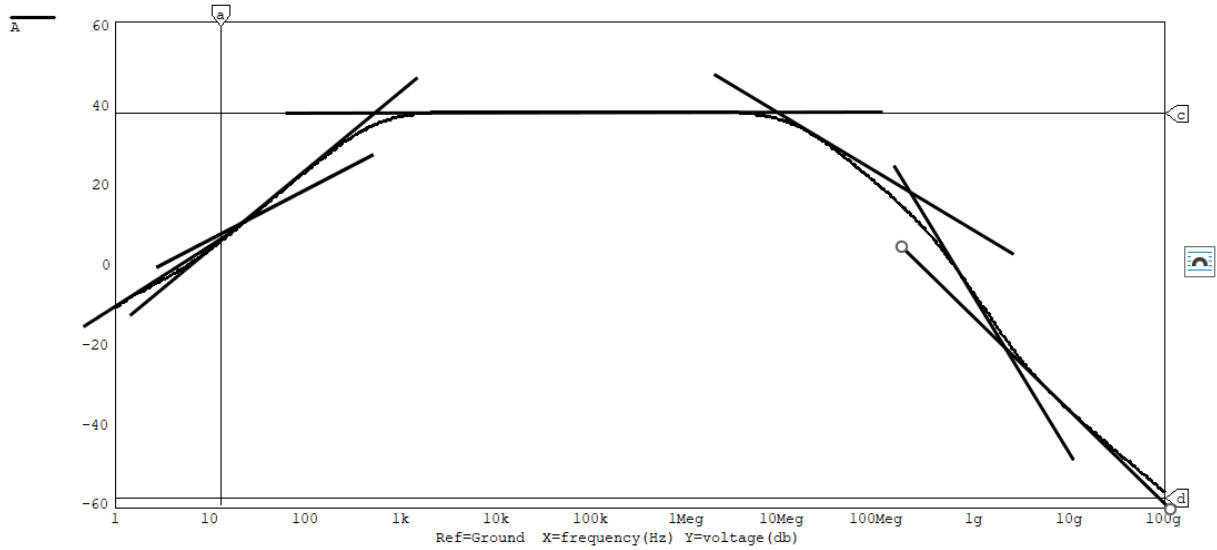


Plot 6: Linear Interpolation for Measuring poles and zeros

	$\omega_{LZ1}$	$\omega_{LZ2}$	$\omega_{LZ3}$	$\omega_{LP1}$	$\omega_{LP2}$	$\omega_{LL3}$	$\omega_{HP1}$	$\omega_{HP2}$
<b>Calculated</b>	0	0	3.701Hz	0.384Hz	1.560Hz	607.75Hz	15.79MHz	34.38MHz
<b>Measured</b>	0	0	4.502Hz	0.557Hz	2.758Hz	690.78Hz	11.67MHz	40.1Mhz

Next, we repeat this process for a 2N4401 transistor, and obtain the poles and zeroes location. by plotting and taking the linear approximation, then by calculations. The same methods are used as for 2N3904 above.

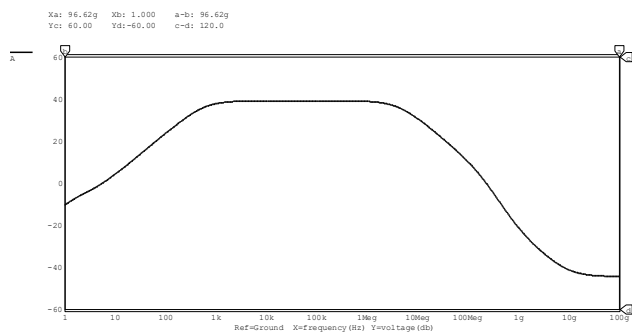

Plot 8: Magnitude Bode Plot for 2N4401

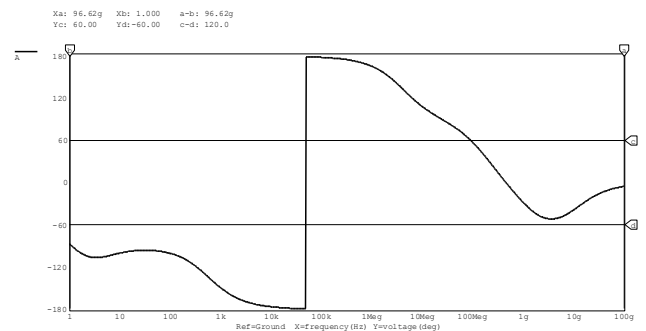


Plot 7: Phase Bode Plot for 2N4401


	$\omega_{LZ1}$	$\omega_{LZ2}$	$\omega_{LZ3}$	$\omega_{LP1}$	$\omega_{LP2}$	$\omega_{LL3}$	$\omega_{HP1}$	$\omega_{HP2}$
<b>Calculated</b>	0	0	5.29Hz	0.491Hz	5.81Hz	3.9kHz	105.2MHz	176MHz
<b>Measured</b>	0	0	6.32Hz	0.524Hz	6.69Hz	4.1kHz	112.3MHz	190MHz

## B. Mid Band Frequency

As we can observe from the Plot 5, the midband frequency ranges from 1kHz to 10Mhz. We choose 20kHz as our midband Frequency to

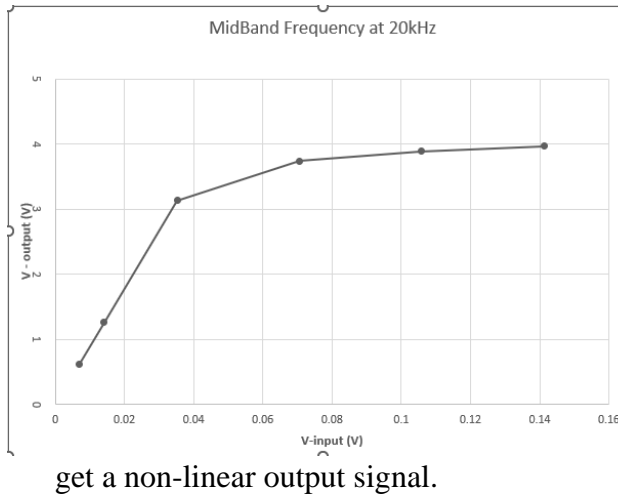

Plot 10: Transfer Curve for 2N3904

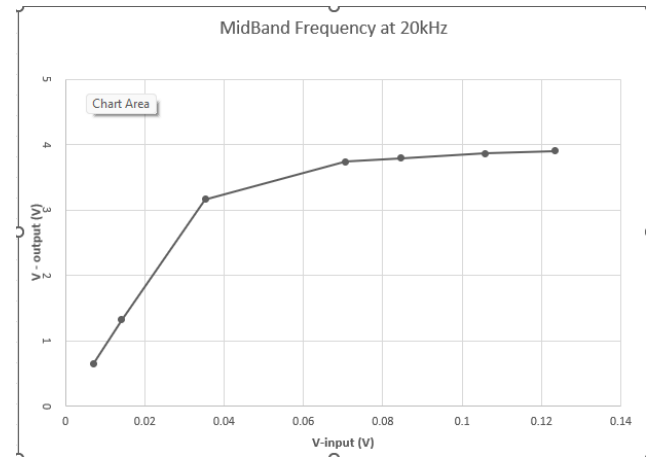

Plot 9: Transfer Curve for 2N4401

## C. INPUT IMPEDENCE

Measured Using *CircuitMaker*:

$$R_{input} = \frac{V_B}{I_{input}}$$

$$2N3904: Z_{input} = \frac{V_B}{I_{input}} = \frac{4.79 V}{5.36 mA} = 893.799 \Omega$$

$$2N4401: Z_{input} = \frac{4.86 V}{5.630 mA} = 863.23 \Omega$$

Calculated:

$$2N3904: Z_{input} = R_{B1} || R_{B2} || r_{\pi} = 2.867 k\Omega$$

$$2N4401: Z_{input} = 2.395 k\Omega$$

#### D. OUTPUT IMPEDENCE

Measured Using *CircuitMaker*:

$$R_{input} = \frac{V_c}{I_{out}}$$

$$2N3904: Z_{input} = \frac{4.080 V}{1.582 mA} = 2.58 k\Omega$$

$$2N4401: Z_{input} = \frac{4.039 V}{1.560 mA} = 2.59 k\Omega$$

Calculated:

$$2N3904: Z_{input} = R_C || R_L = 2.55 k\Omega$$


$$2N4401: Z_{input} = 2.55 k\Omega$$

#### E. Best Performance Transistor


I believe 2N3904 is better as it can handle high currents and gets a linear output domain at much lower peak amplitude as compared to 2N4401.

## PART 3


A.

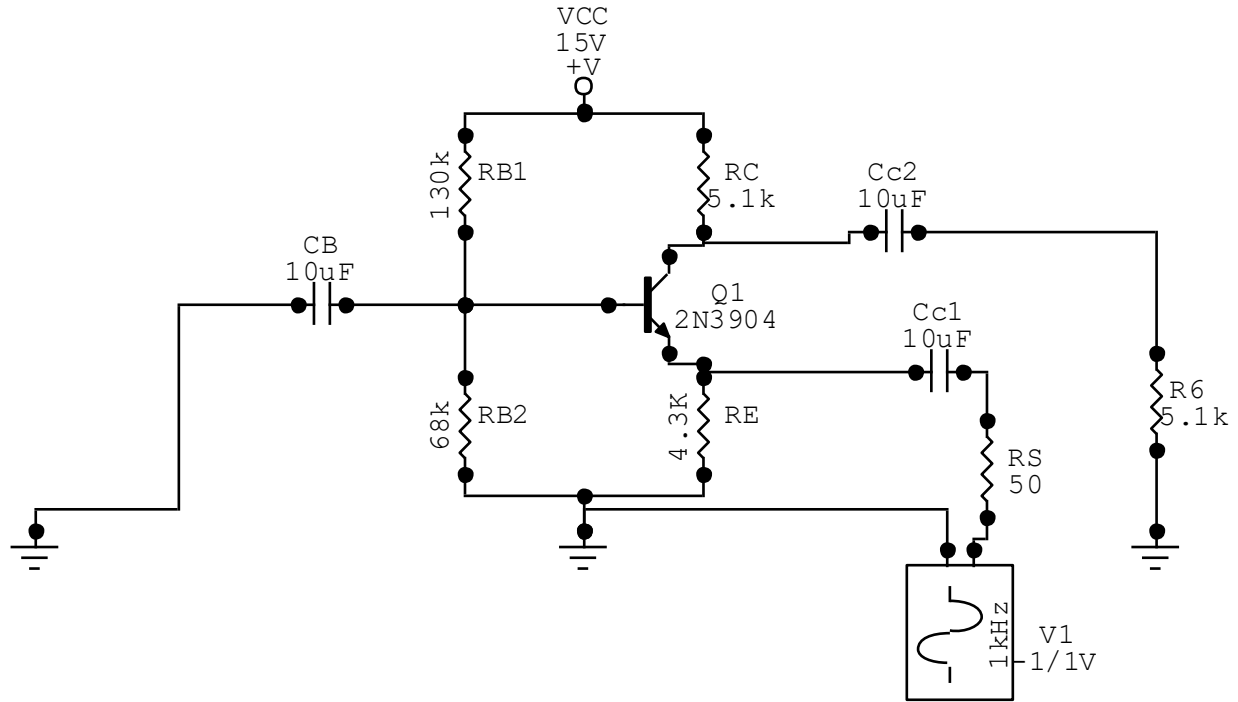

Circuit 9: Common Base Amplifier

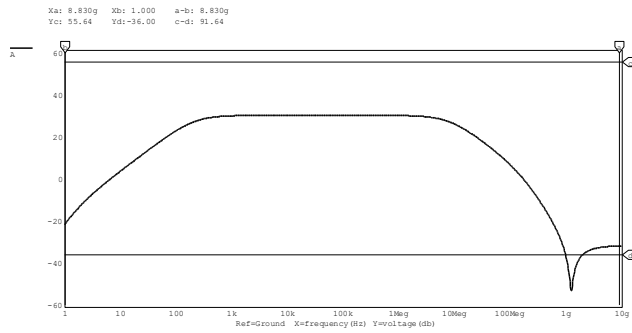

Plot 12: Magnitude Bode Plot for CB Amplifier

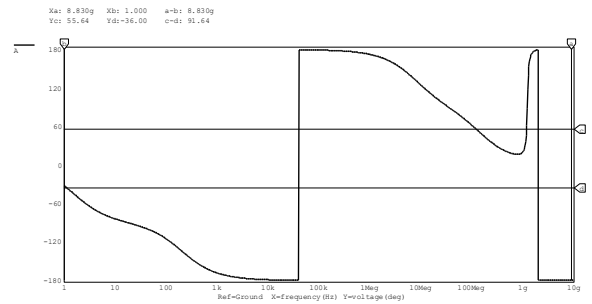

Plot 11: Phase Bode Plot for CB Amplifier

$$g_m = \frac{993.3\mu A}{0.025V} = 0.039732 S$$

$$V_{CB} = 5.058 V$$

$$V_{BE} = 0.601 V$$

$$C_{\pi} \approx 2 * C_{JE} + TF * g_m = 74.77360 pF$$

$$C_{\mu} \approx \frac{C_{JC}}{\left(1 + \frac{V_{CB}}{V_{JC}}\right)^{M_{JC}}} = 7.73544 pF$$

$$k = -g_m(R_C || R_L) = -101.316$$

$$r_{\pi} = 4.17 k\Omega$$

$$\omega_{LZ3} = \frac{1}{R_{BB}C_B} = 0.357 \text{ Hz}$$

$$\omega_{LP2} = \frac{1}{(R_L + R_C)C_{C2}} = 1.5603 \text{ Hz}$$

$$\omega_{LP1} = \frac{1}{C_B((R_E(1 + \beta) + r_\pi)||R_{BB})} = 0.3781 \text{ Hz}$$

$$\omega_{LP3} = \frac{1}{\left(R_E||\frac{r_\pi}{1 + \beta} + R_S\right)C_{C1}} = 535.03 \text{ Hz}$$

By shorting all the low frequency capacitors,


$$\omega_{HP1} = \frac{1}{\left(R_{BB}||R_S C_\pi||\frac{r_\pi}{1 + \beta}\right)} = 42.569 \text{ MHz}$$

$$\omega_{HP2} = \frac{1}{(R_L||R_C)C_\mu} = 8.06853 \text{ MHz}$$

	$\omega_{LZ1}$	$\omega_{LZ2}$	$\omega_{LZ3}$	$\omega_{LP1}$	$\omega_{LP2}$	$\omega_{LL3}$	$\omega_{HP1}$	$\omega_{HP2}$
<b>Calculated</b>	0	0	0.357Hz	0.3781Hz	1.560Hz	535.03Hz	42.569MHz	8.065MHz
<b>Measured</b>	0	0	0.98 Hz	0.42 Hz	3.1 Hz	550.2 Hz	45.76 MHz	9.12 MHz

## B. Midband Frequency

From the bode plot, midband frequency ranges from 1kHz to 1MHz. I choose 10kHz to get nonlinear transfer function graph. It is observed that near 70 mV, the output domain starts to get non - linear

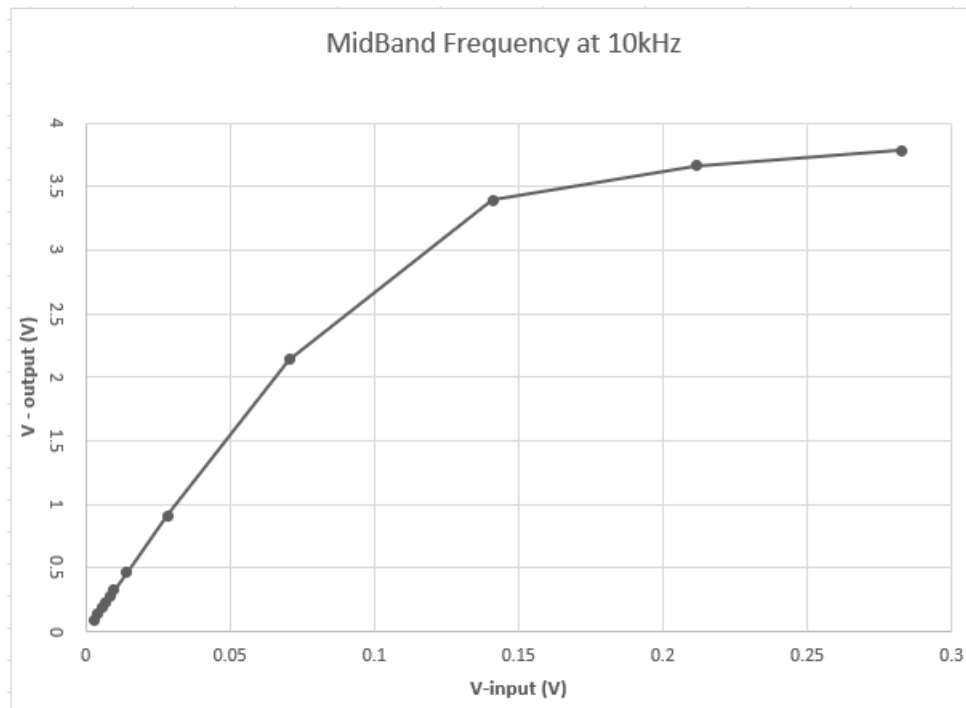

Plot 13: Transfer Curve for 2N2222A

### C. Input Impedance

$$\text{Measured: } R_{in} = \frac{V_{in}}{I_{in}} = \frac{704.9 \text{ mV}}{5.755 \text{ mA}} = 122.48 \Omega$$

$$\text{Calculated: } R_{in} = R_E \parallel \frac{r_{\pi}}{1+\beta} = 35.05 \Omega$$

### D. Output Impedance

$$\text{Measured: } R_{out} = \frac{4.002 \text{ V}}{1.553 \text{ mA}} = 2.576 \text{ k}\Omega$$

$$\text{Calculated: } R_{out} = R_C \parallel R_L = 2.55 \text{ k}\Omega$$

Both values are very close.

## Conclusion

The goal of this project was to model, bias, and test different types of transistor amplifiers, including Common-base and Common-emitter amplifiers. The first step involved analyzing the characteristics of the transistors at specific voltages and currents, and comparing the results to both calculated values and data from the transistor's datasheet. To ensure that the transistors were operating correctly, they were biased to their DC operating point using a variety of methods, including measurement and the use of the  $\frac{1}{3}$  rule with standard resistors. The Bode plot was then analyzed to identify the locations of poles and zeroes, and any discrepancies between calculated and measured values were noted. The project also included an investigation into the effects of large signals on small signal models, which provided valuable insight into the performance of the approximate transistor models.

## References

1. ELEC 301 Course Notes.
2. 2N2222A Datasheet <https://www.st.com/resource/en/datasheet/cd00003223.pdf>
3. 2N2222A Datasheet Plots <https://web.mit.edu/6.101/www/reference/2N2222A.pdf>
4. 2N3904 Datasheet <https://www.onsemi.com/pdf/datasheet/2n3903-d.pdf>
5. 2N4401 Datasheet <https://www.onsemi.com/pdf/datasheet/2n4401-d.pdf>